

# North South University ECE

Experiment No: 5

Experiment Title: Design of a Register File

Course Code: CSE332L

Course Name: Computer Organization & Architecture Lab

Name & ID: Md. Ishtiaq Ahamed Fahim 2012518642

Date of Experiment: 7.4.2022

Date of Submission: 10.4.2022

Objective:

- Design a register file that is 16 bit wide. Label properly the inputs/outputs/selections
- Design the interfacing for reading data from any of those registers.
- Design the interfacing for writing data to any of those registers. Make sure it has to write to control signal

Apparatus:

Logisim Tool

Block Diagram:

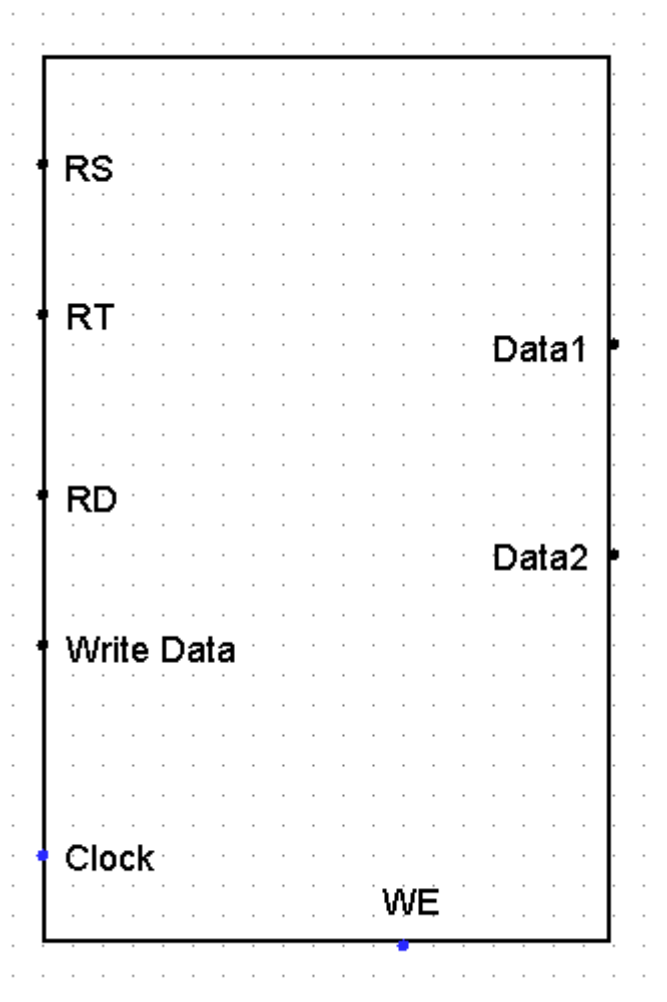


Fig-1: register 16 bit wide

Circuit diagram:

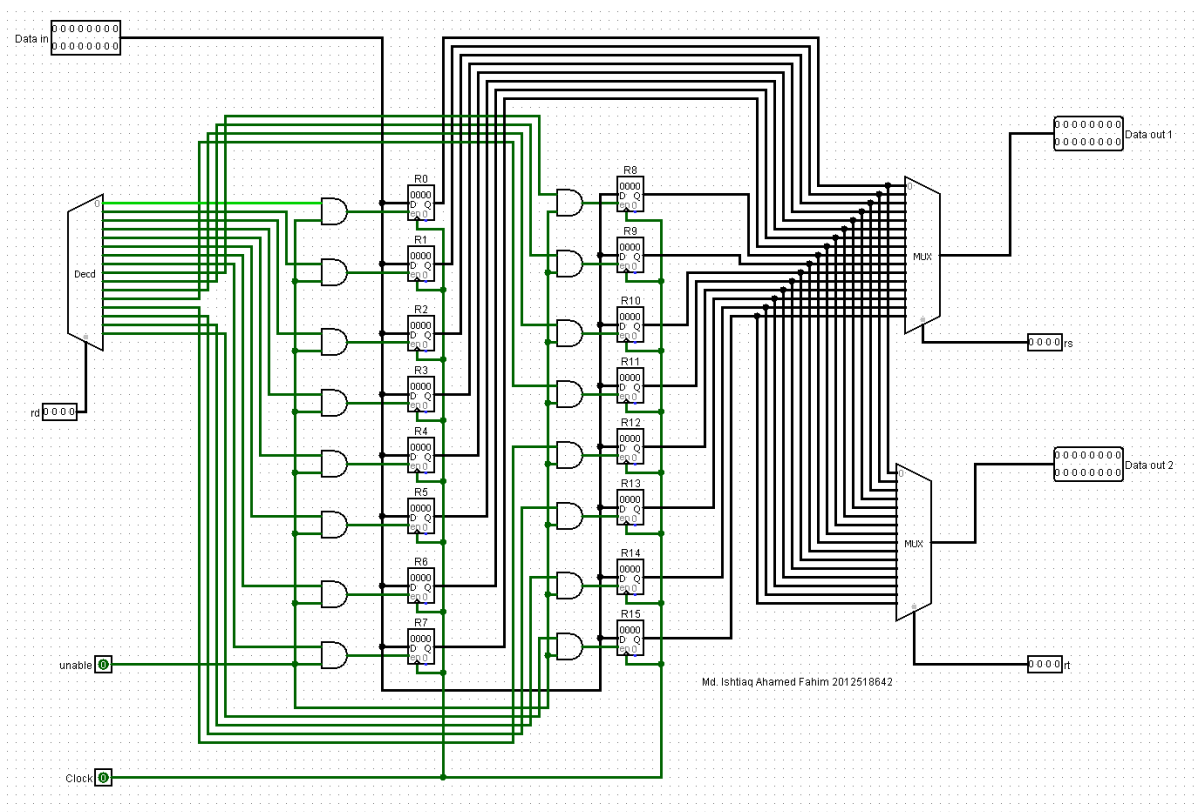


Fig-2: 4-bit by 4-bit Binary Multiplication Unit (Circuit diagram)

## Discussion:

We learned how to create a 16 bit wide register and understand how rs and rt access the read part of the register and rd control the write part with proper select bit in following case and how clock play role in it and to be enable or disable the unit.